

Practical Exercise 2

Circuit A

1. 100 ohms

2. 1.25A

3. 1.25A

4. $R_1 = 25.00 \text{ V}$

$R_2 = 37.50 \text{ V}$

$R_3 = 62.50 \text{ V}$

5. $R_1 = 31.25 \text{ W}$

$R_2 = 46.88 \text{ W}$

$R_3 = 78.13 \text{ W}$

Circuit B

1. 12.5 ohms

2. 10A

3. $R_1 = 6.25 \text{ A}$

$R_2 = 1.25 \text{ A}$

$R_3 = 2.50 \text{ A}$

4. 125V

5. $R_1 = 781.25 \text{ W}$

$R_2 = 156.25 \text{ W}$

$R_3 = 312.50 \text{ W}$